

# www.mbsm.pro , PICTURE, How to Make, Blinking Indicator, With relay 6v , Condensor 1000uf , battery 9v , and a simple led

Category: electronique, Tester ok

written by mahdi miled | 3 January 2019

www.mbsm.pro , How to Make, Blinking Indicator, With relay 6v , Condensor 1000uf , battery 9v , and a simple led

mbsm-group-dot-pro-pictures-Blinking.png (385 KB)



mbsm-group-dot-pro-pictures-Blinking.png (351 KB)



mbsm-group-dot-pro-pictures-Blinking1.png (312 KB)



mbsm-group-dot-pro-pictures-Blinking1.png (282 KB)



mbsm-group-dot-pro-pictures-Blinking2.png (330 KB)



mbsm-group-dot-pro-pictures-Blinking2.png (295 KB)



mbsm-group-dot-pro-pictures-Blinking4.png (236 KB)



mbsm-group-dot-pro-pictures-Blinking4.png (213 KB)

