# Mbsm.pro, Conversion circuit, from $220\ v$ to $12\ v$ / $1\ A$ , to operate a, DC12V, fan, in the refrigerator

Category: electronique

written by rober us | 16 January 2024



Private Picture Copyright: WWW.MBSM.PRO




## 1. AC-DC Adapter:


- Convenient and compact: Pre-built, plug-and-play solution.
- Power rating: Choose an adapter with a power rating sufficient for your fan's wattage.
- Image:



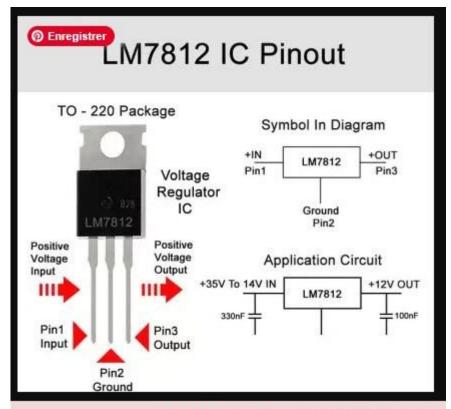- 2. Transformer and Rectifier Circuit:
- Step-down transformer: Reduces 220V AC to a lower AC voltage (e.g., 12V AC).
- Rectifier circuit: Converts AC to DC.
- Capacitor: Smoothes out voltage fluctuations.
- Image:


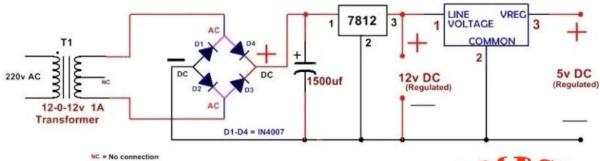
# 220/230v AC to 12V DC, 5V DC Converter Circuit Using Bridge Rectifier



230v ac to 12v dc and 5v dc Regulated Power Converter



7805

Private Picture Copyright: WWW.MBSM.PRO

- 3. Switching Power Supply (SMPS):
- High efficiency: Typically over 80%, reducing energy waste.
- Smaller size: Compared to linear power supplies.
- Available as pre-built modules or DIY kits:
- Image:



### **Key Considerations:**

- Fan's power requirements: Ensure the converter can supply the necessary current.
- Safety: Implement proper insulation and grounding for AC connections.
- **Heat dissipation:** Consider heat sinks for transformers or power supplies, especially for high-power fans.
- **Placement:** Avoid placing the converter in areas with high moisture or condensation.
- **Professional installation:** Recommended for those unfamiliar with electrical work.

#### Additional Tips:

- Fuse: Add a fuse to the circuit for added protection against short circuits.
- Switch: Include a switch to easily turn the fan on and off.
- LED indicator: Add a LED indicator to show when the converter is powered on.